

Programmable-Gain Amp Uses Arbitrary-Attenuation Step Ladder

Victor Koren

Tioga Technologies, 32 Nachalat Yitzhak St., Tel Aviv 67448 Israel; +972 3 607 0333; fax: +972 3 607 0334; e-mail: info@tiogatech.com

CIRCLE 520

The R-2R ladder, a well known resistor topology, is often used to implement a current or voltage 6-dB step attenuator. By appropriately scaling the resistor values, this network also can be modified to provide any desired attenuation.

The modified resistor ladder uses three different resistor values (see the figure). A short algebraic manipulation can show that:

$$\text{Step attenuation (dB)} = 20 \log [R3/(R1 + R3)]$$

$$R_{IN} = R1 + R3$$

$$R2 = R3 (1 + R3/R1)$$


If $R1 = R3$, then $R2 = 2 \times R1$. In this case, the R-2R network provides a 6-dB step attenuation.

To determine the resistor values for a specific step attenuation and input resistance, use the formulas:

$$K = 10^{[\text{step attenuation (dB)}/20]}$$

(Note that the step attenuation (dB) value should be negative!)

$$R1 = R_{IN} (1 - K)$$

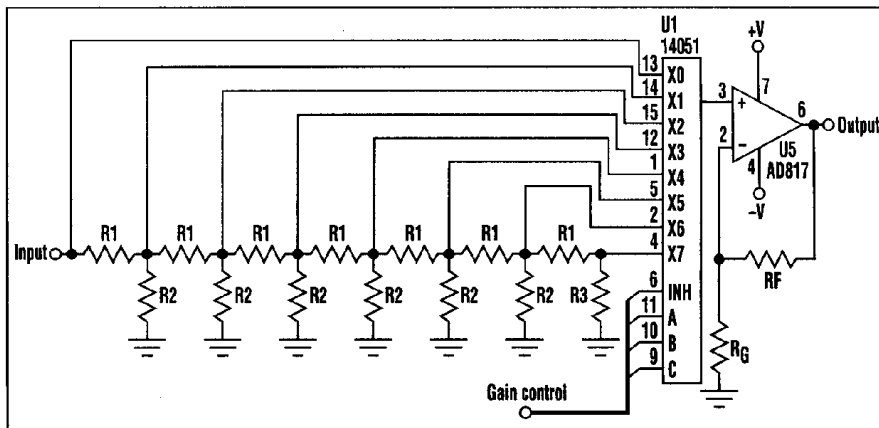

This wide-bandwidth, low-distortion programmable gain amplifier (PGA) is built using low-cost standard devices, eliminating the need for an expensive programmable-gain amp IC.

$$R2 = R_{IN} \times K / (1 - K)$$

$$R3 = 0.8414 \times 500 = 420.7 \Omega$$

$$R3 = K \times R_{IN}$$

For example, to implement a resistor ladder with a -1.5 -dB step attenuation and $500\text{-}\Omega$ input impedance:

$$K = 0.8414$$

$$R1 = 500 (1 - 0.8414) = 79.3 \Omega$$

$$R2 = 500 \times 0.8414 / (1 - 0.8414) = 2653 \Omega$$

There are a couple of interesting points to observe about the PGA circuit. A standard CMOS analog switch is used to connect the attenuated signal to the noninverting input of the op amp, which has a high input impedance. Since the current through the switch is negligible, low attenuation and distortion is achieved. A wide-bandwidth (video-bandwidth), low-distortion PGA is created through the use of very low-cost standard devices. □